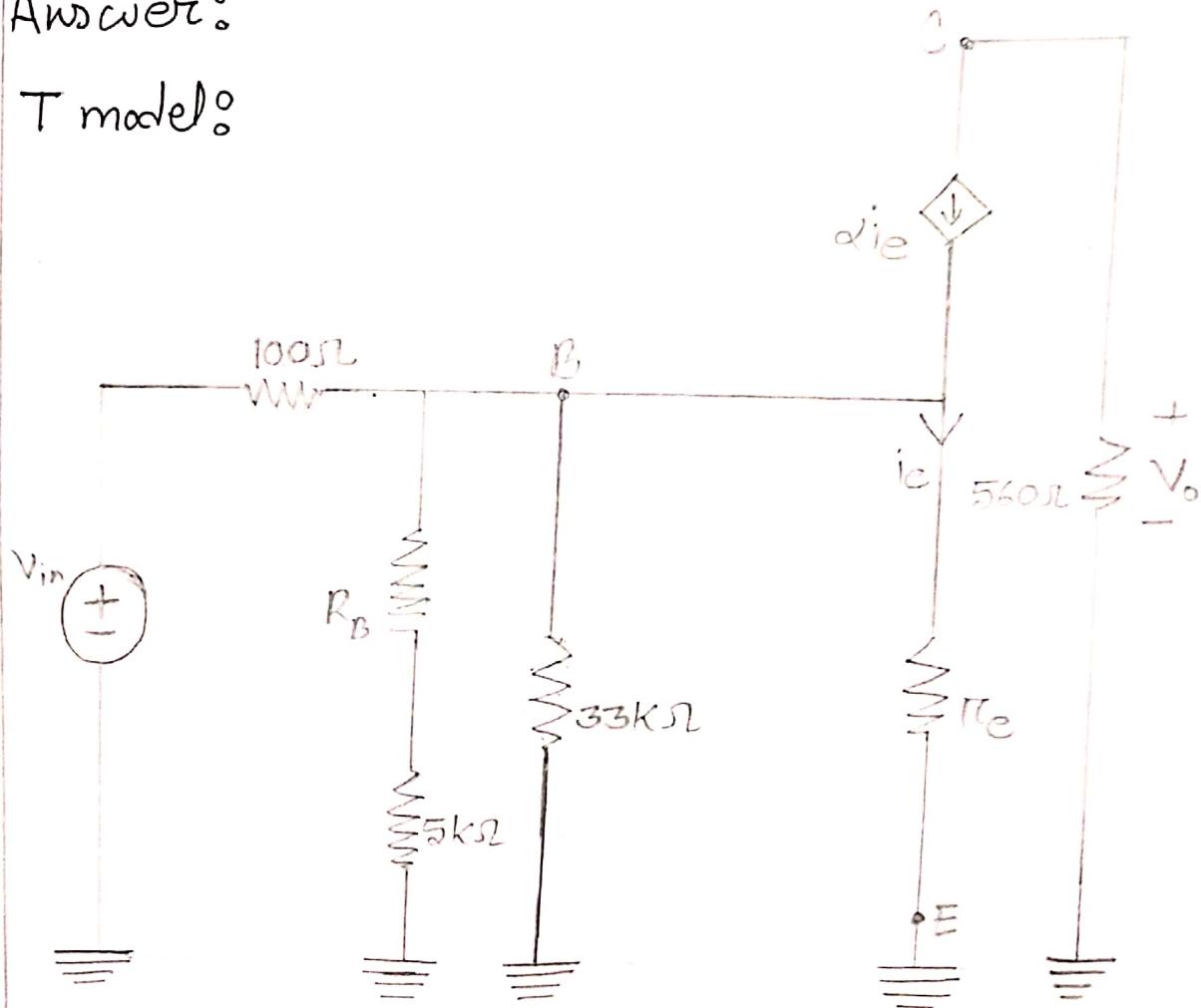


Prelab work:


1. Draw the small signal equivalent circuits of the CE Amplifier circuit.

Answer:

T model:




π model

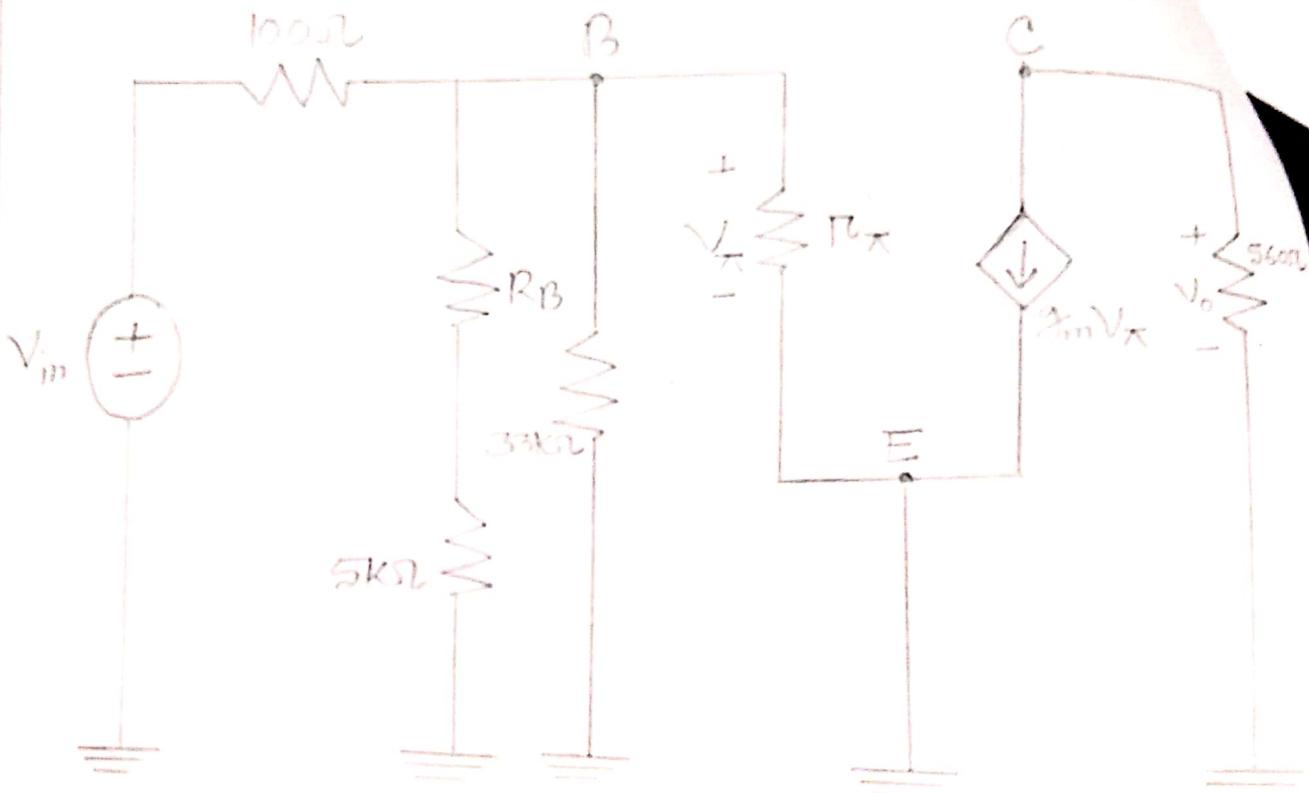

2. Obtain voltage gain

2. Obtain an expression for the voltage gain ($\frac{V_o}{V_{in}}$).

Answer:

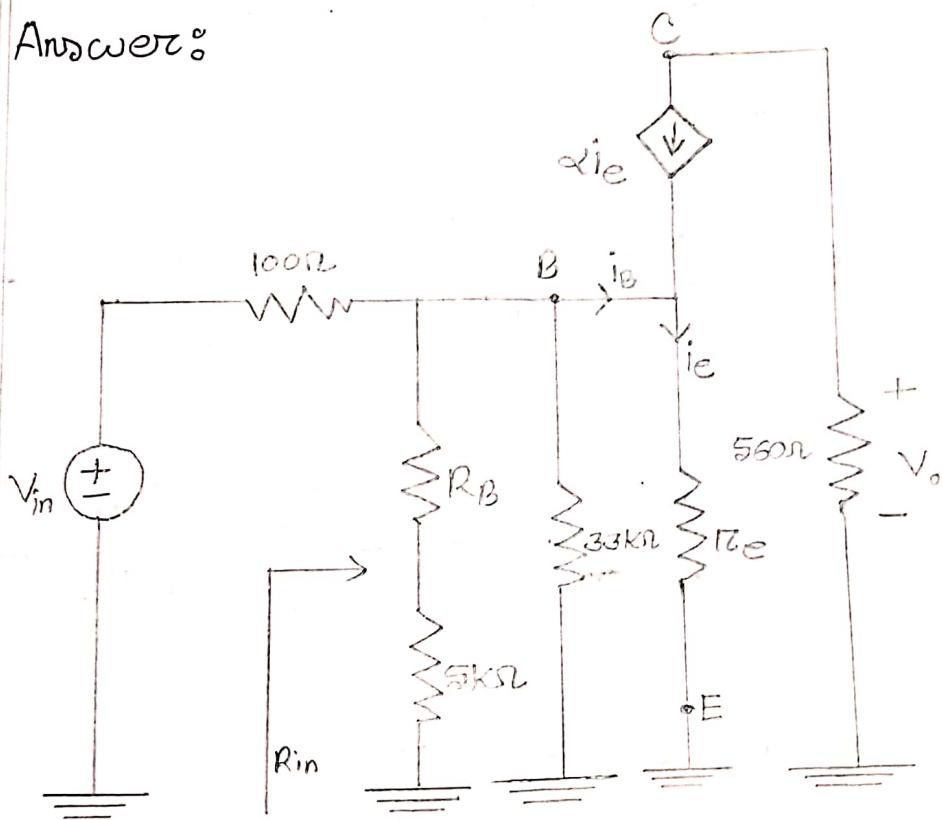

$$V_0 = -560 \alpha^{\frac{1}{3}} e \quad \dots \text{(i)}$$

$$V_b = i_e \tau e \dots \text{ (ii)}$$

$$R_{jn} = \left(\frac{1}{33 \times 10^3} + \frac{1}{R_B + 5 \times 10^3} + \frac{1}{R_e} \right)^{-1}$$

$$V_b = \frac{\left(\frac{1}{3.3 \times 10^3} + \frac{1}{R_B + 5 \times 10^3} + \frac{1}{r_e}\right)^{-1}}{100 + \left(\frac{1}{3.3 \times 10^3} + \frac{1}{R_B + 5 \times 10^3} + \frac{1}{r_e}\right)^{-1}}, \quad V_{in} \text{ - (b)}$$

Remove gain.
 $CE = 10$

from (i) and (ii),

$$\frac{V_o}{V_b} = - \frac{560\alpha}{r_e} \quad \dots (iv)$$

from (iii) and (iv),

$$A_v = \frac{V_o}{V_{in}} = \frac{\left(\frac{1}{33 \times 10^3} \frac{1}{R_B + 5 \times 10^3} \frac{1}{r_e} \right)^{-1}}{100 + \left(\frac{1}{33 \times 10^3} \frac{1}{R_B + 5 \times 10^3} \frac{1}{r_e} \right)^{-1}} \times \frac{-560\alpha}{r_e}$$

$$= \frac{-560\alpha \left(\frac{1}{33 \times 10^3} + \frac{1}{R_B + 5 \times 10^3} + \frac{1}{r_e} \right)^{-1}}{r_e \left\{ 100 + \left(\frac{1}{33 \times 10^3} + \frac{1}{R_B + 5 \times 10^3} + \frac{1}{r_e} \right)^{-1} \right\}}$$

or, $R_{in} = (1+\beta) r_e$

$$A_v = \frac{-560\alpha (1+\beta) r_e}{r_e \left\{ (1+\beta) r_e + 100 \right\}}$$


$$= \frac{-560\alpha (1+\beta)}{(1+\beta) r_e + 100}$$

EXPT. NO.

O3

NAME OF THE EXPERIMENT
Diode

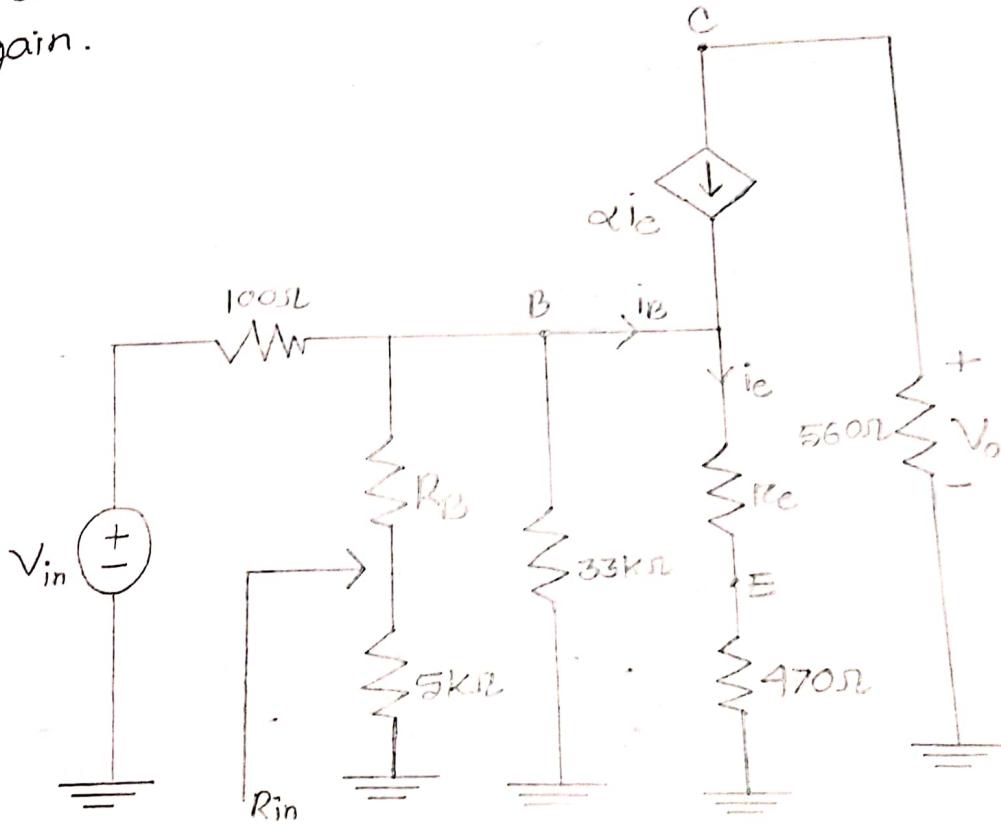Remove $C_E = 10\text{MF}$ and obtain voltage gain.



$$V_o = -560\alpha i_e \quad \dots (i)$$

$$V_b = i_e (\tau_e + 470) \quad \dots (ii)$$

$$R_{in} = \left(\frac{1}{33 \times 10^3} + \frac{1}{R_B + 5 \times 10^3} + \frac{1}{\tau_e + R_e} \right)^{-1}$$

$$V_b = \frac{\left(\frac{1}{33 \times 10^3} + \frac{1}{R_B + 5 \times 10^3} + \frac{1}{\tau_e + R_e} \right)^{-1}}{100 + \left(\frac{1}{33 \times 10^3} + \frac{1}{R_B + 5 \times 10^3} + \frac{1}{\tau_e + R_e} \right)^{-1}} V_{in} \quad \dots (iii)$$

$$\frac{\frac{0.1 + (1+B)}{(1+B)(R_e + 470) + 100}}{-560\alpha(1+B)} =$$

$$\frac{\frac{(R_e + R_B)(1+B)(R_e + 470) + 100}{(1+B)(R_e + 470)}}{-560\alpha(1+B)(R_e + 470)} = \therefore A_V =$$

$$R_{in} = (1+B)(R_e + 470)$$

$$A_V = \frac{V_o}{V_{in}} = \frac{-560\alpha \left(\frac{1}{R_B + 510} + \frac{1}{R_e + 470} \right)}{\frac{1}{R_B + 510} + \frac{1}{R_e + 470}}$$

from (iii) and (iv)

$$\frac{R_e + 470}{560\alpha} = -\frac{V_o}{V_{in}}$$

from (i) and (ii)

obtain an expression for output resistance R_o .

Answer: By the small signal equivalent circuit $R_o = 560\Omega$

Report:

Plot the gain in dB as a function of frequency in a semi log paper.

Answer: Different gain in different frequency was measured during the experiment.

Frequency Hz	Gain (dB) ($\log A_V$)
50	3.01
100	3.97
200	6.98
500	10
800	12.50
1000	13.01
2000	16.98
5000	16.98

lower cutoff frequency: 200 Hz

Higher cutoff frequency: 5000 Hz

mid band gain: 16.98 dB

- Q. What is the input impedance, output impedance and phase relationship between input and output for CE amplifier and comment on them.

Ans: Input impedance: input impedance is the impedance seen by the source.

Eff in the ratio of voltage current flowing in. $R_{in} = \frac{V_b}{I_b}$
from experiment $R_{in} = 2.3\Omega$

Output impedance: The output ~~the~~ impedance is the ratio of the output voltage and the output current.

from experiment $R_o = 622\pi$

Phase relationship: The phase difference in CE amplifier is 180° . It was noticed from the experiment.

Q. What is the function of bypass capacitor and dc blocking capacitor?

Answer:

Bypass capacitor: The capacitor is parallel with the emitter resistor in bypass capacitor. It is called bypass capacitor because in high frequency the AC current bypasses the R_E and flows through the capacitor. It works like a short circuit then. An high frequency $X_C < R_E$. But in low frequency it works like an open circuit. Moreover it decreases the input impedance and increases the voltage gain.

DC blocking capacitor: The capacitors in series with V_{in} and V_o are called DC blocking capacitors or coupling capacitors. It blocks the DC part of the signal from going to leave. It also blocks the DC part of the output at V_o . Only the AC signal passes through capacitors.

~~Ques~~
what is the advantage and dis-
advantage of common emitter am-
plifier?

Answer:

Advantages:

If has very low input impedance. The current and voltage gains are very good. If has wide frequency response and large bandwidth. If's power gain is the highest.

Disadvantages:

If has a high output resistance. If's voltage gain is not stable. If responds bad to very high frequencies.

6. Using measured value of R_B , calculate voltage gain from given expressions for $B=75$. If value of g_m and r_π required, determine g_m and r_π from DC analysis for the circuit.

Answer: $B=75 \therefore \alpha = 0.99$

$$V_{CC} = 15 \text{ V} \quad R_B = 400 \Omega$$

$$V_{CE} = 7.6 \text{ V}$$

$$I_C R_C + V_{CE} = V_{CC}$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{CE}}{BR_C}$$

$$= \frac{15 - 7.6}{75 \times 560}$$

$$= 1.76 \times 10^{-3} \text{ A}$$

$$\therefore I_E = (B+1) I_B = 0.013 \text{ A}$$

$$\therefore r_e = \frac{V_t}{I_E}$$

$$= \frac{25 \times 10^{-3}}{0.013}$$

Clipping
from PB, QD

while C_E is connected

QD

$$R_e = 1.92 \Omega$$

while C_E is disconnected

$$A_V = \frac{-560 \times 99 \left(\frac{1}{33 \times 10^3} + \frac{1}{400+5 \times 10^3} + \frac{1}{1.92} \right)^{-1}}{1.92 \left\{ 100 + \left(\frac{1}{33 \times 10^3} + \frac{1}{400+5 \times 10^3} + \frac{1}{1.92} \right)^{-1} \right\}}$$
$$= -5.437$$

while C_E is disconnected

$$A_V = \frac{-560 \times 99 \left(\frac{1}{33 \times 10^3} + \frac{1}{400+5 \times 10^3} + \frac{1}{1.92+970} \right)^{-1}}{(1.92+970) \left\{ 100 + \left(\frac{1}{33 \times 10^3} + \frac{1}{400+5 \times 10^3} + \frac{1}{1.92+970} \right)^{-1} \right\}}$$
$$= -0.95$$


$$V_{CC} = 15V$$

$$V_{CE} = 7.6V$$

$$V_{IN} = 10mV$$

$$V_o = 6.5V$$
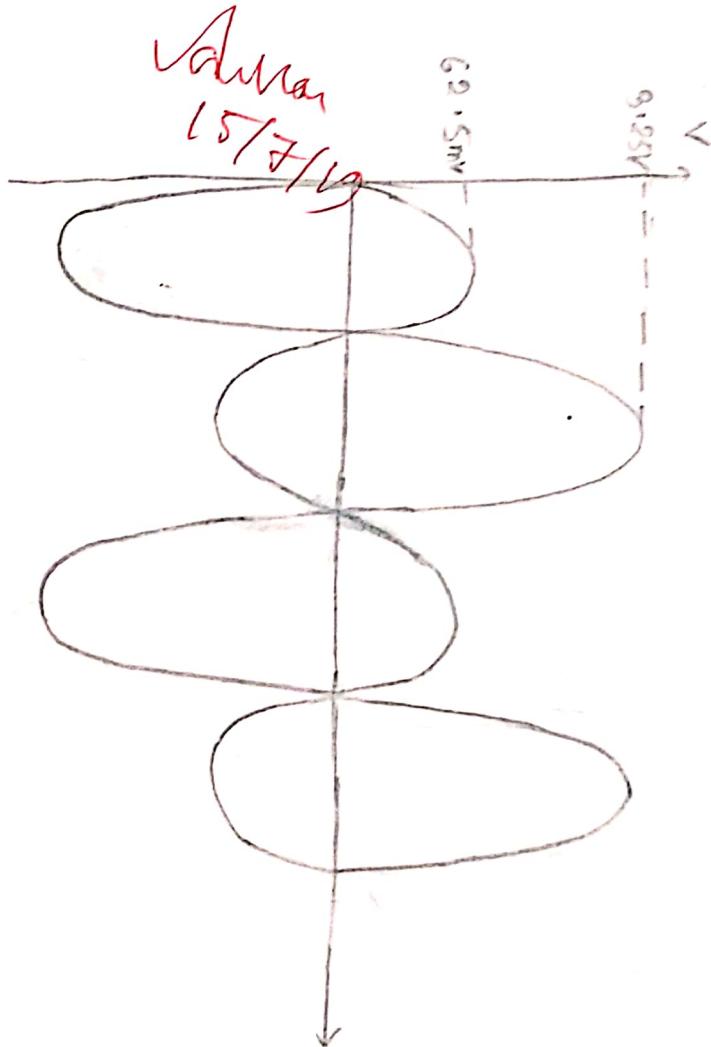
$$A_V = \frac{V_o}{V_{IN}} = \frac{6.5}{10 \times 10^{-3}} = 650$$



4. Potentiometer $0.4k\Omega$

5. Peak voltage = $0.5mV$

$$6. \text{ Gain} = \frac{10mV}{5.55mV} = 1.8$$

$$7. V_{IN} = 100mV; \text{ Gain} = 100 \times 10^{-3} = 100$$

$$V_{OUT} = 100 \times 0.1 \text{ V} = 10V$$

Ex

100 Hz,

$$V_{out} = 0.25 V \quad f_{cain} = 2.5$$

$$V_{in} = 100 mV$$

200 Hz,

$$V_{out} = 0.5 V \quad f_{cain} = 5$$

$$V_{in} = 100 mV$$

500 Hz,

$$V_{out} = 1 mV \quad f_{cain} = 10$$

$$V_{in} = 100 mV$$

800 Hz, $V_{out} = 1.8 V \quad f_{cain} = 18$

$$V_{in} = 100 mV$$

1000 Hz, $V_{out} = 2 V \quad f_{cain} = 20$

$$V_{in} = 100 mV$$

2000 Hz, $V_{out} = 5 V \quad f_{cain} = 50$

$$V_{in} = 100 mV$$

~~proportion~~ V_{out} =

5000 Hz, $V_{out} = 5 V \quad f_{cain} = 50$

$$V_{in} = 100 mV$$

6000 Hz, $V_{out} = 4 V \quad f_{cain} = 40$

$$V_{in} = 1000 mV$$

7000 Hz, $V_{out} = 3.2 V \quad f_{cain} = 32$

$$V_{in} = 100 mV$$

264 (Elec)

and

$$f_{out} = 2.5 \text{ V}$$
$$V_{in} = 100 \text{ mV}$$

$$f_{out} = 25$$

$$10,000 \text{ Hz}$$
$$V_{out} = 1.8 \text{ V}$$
$$V_{in} = 100 \text{ mV}$$

$$f_{out} = 18$$

1705025, 1705026
1705021, 1705029
13.06.19
Submission: