

display was located. Proper connection (according to Fig. 4)

was made and the output

was observed.

4. Step 3 was repeated by increasing supply frequency to 5 kHz.

Result:


✓

The readings obtained for the circuit diagram in Fig. 2 are as follows:

V_D (v)	V_{dc} (v)	V_R (v)	I_D (Amp)
0.1	0.1	0	0
0.2	0.2	0	0
0.3	0.3	0	0
0.4	0.4	0	0
0.5	0.9	0.5	5×10^{-4}
0.6	6.1	5.8	5.8×10^{-3}
0.7	11.3	10.6	0.0106
0.7	17.1	16.2	0.0162
0.7	25.0	24.6	0.0246


The readings obtained for the circuit diagram
in Fig - 3.

V_D (v)	V_{dc} (v)	V_R (v)	I_D (Amp)
0.5	0.5	0	0
1.0	1.0	0	0
1.5	1.5	0	0
2.0	2.0	0	0
2.5	2.5	0	0
3.0	3.0	0	0
3.5	3.5	0	0
4.0	4.0	0	0
4.5	4.58	0.08	8×10^{-5}
5.0	5.16	0.18	1.8×10^{-4}
5.15	25.0	19.8	0.0198

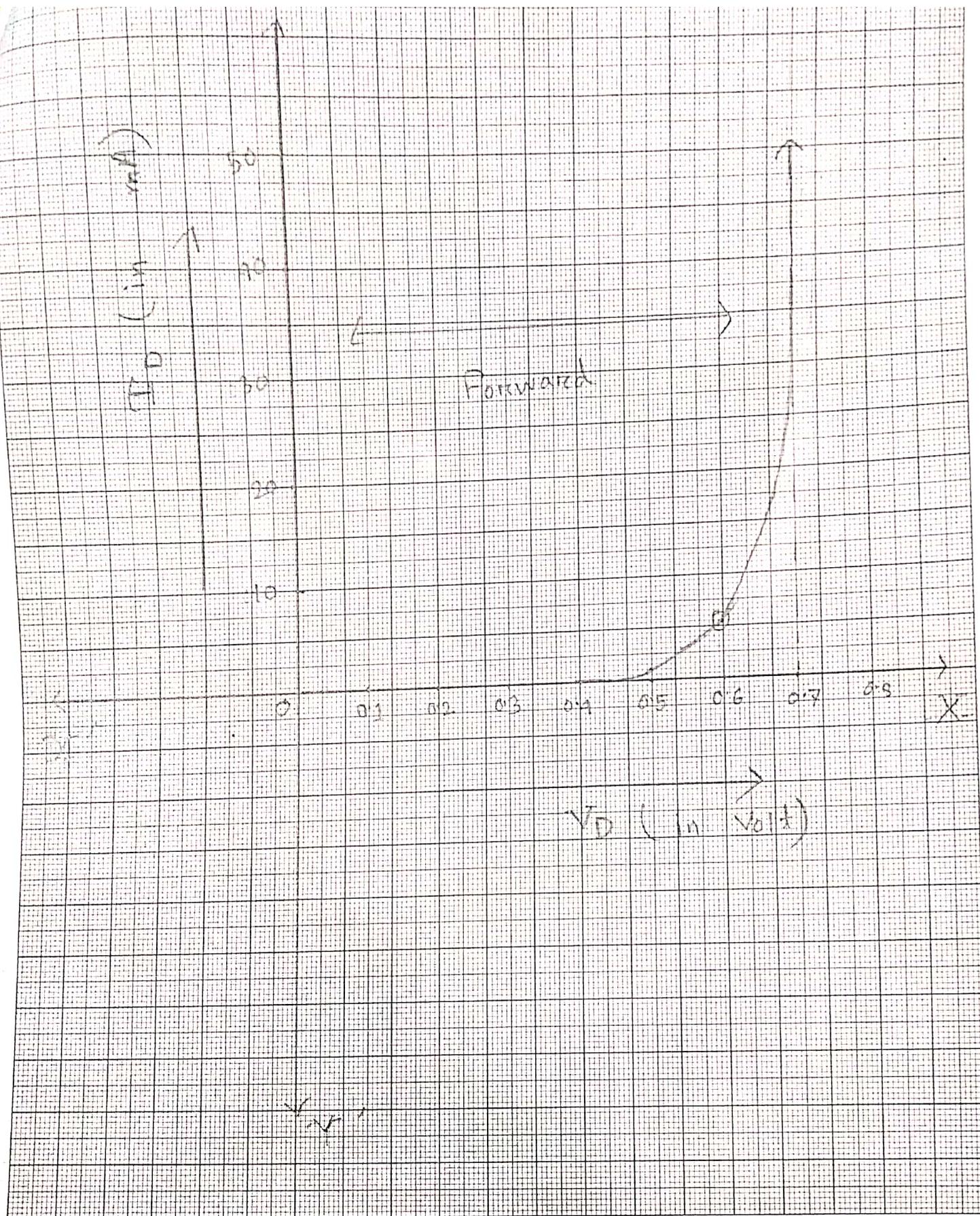

$$10 \times 10^{-3} = 10^{-2}$$


Pn Fig. 3

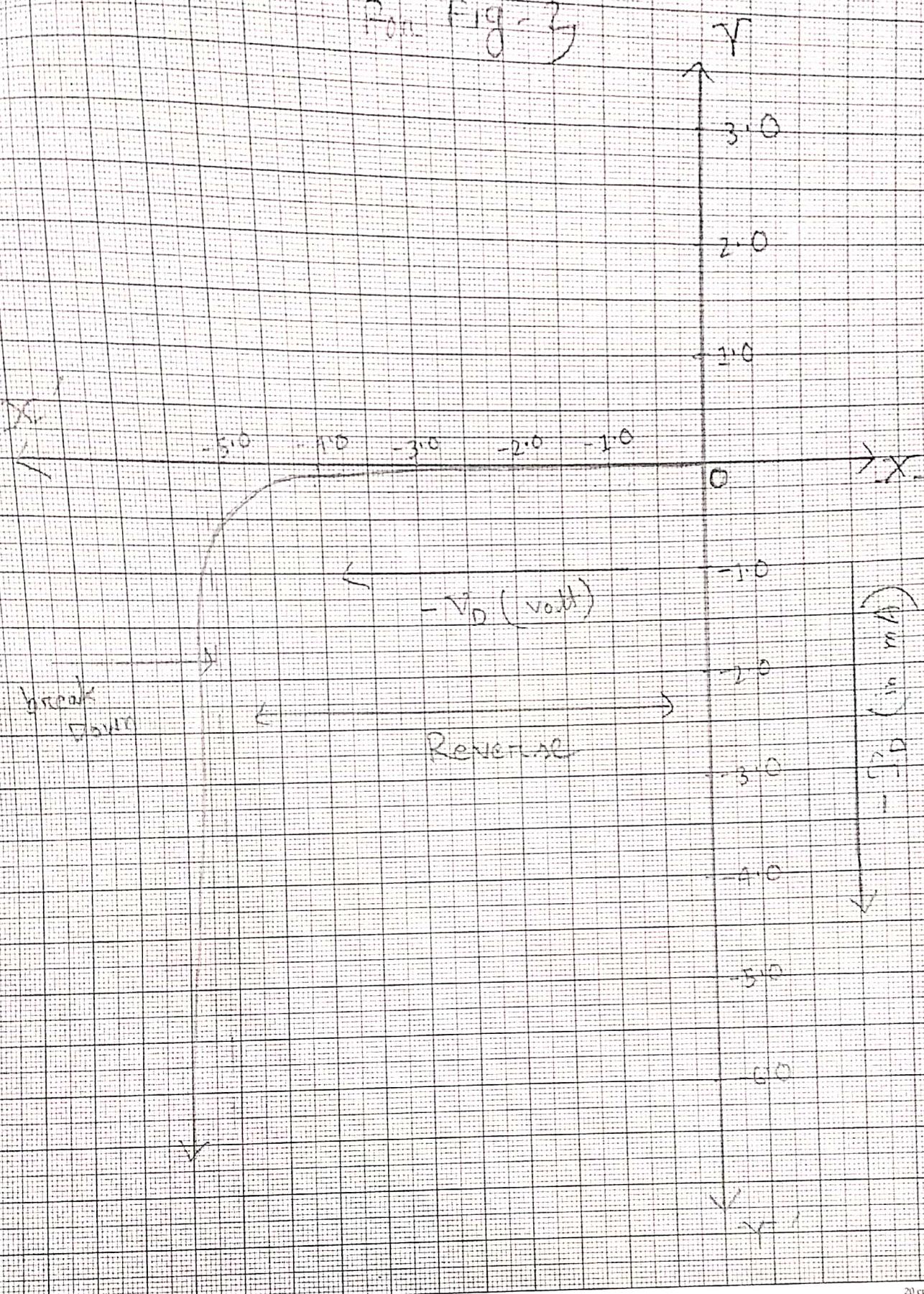

20 cm x 25 cm

$$\mu \cdot R \cdot I \cdot d = \frac{1}{10 \times 10^{-3}} = (2.6 \text{ m}) \rightarrow L$$

Fig. 4

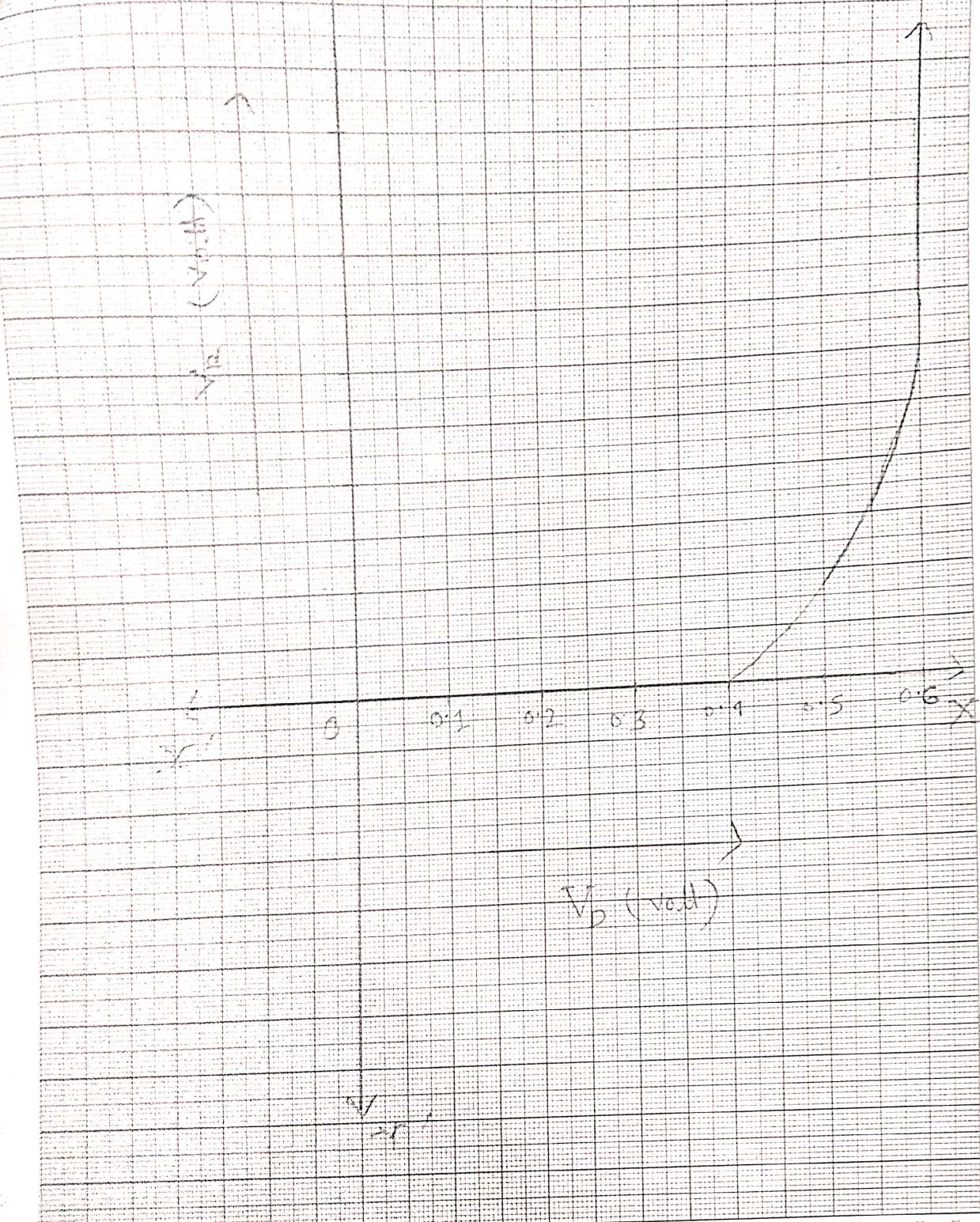
100, $f = 100 \text{ Hz}$ 

20 cm x 25 cm

Academia

$$D.K., n_d = \frac{n \times 0.026}{10 \times 10^{-3}} = (2.6n) \perp 2$$

Form Fig. A

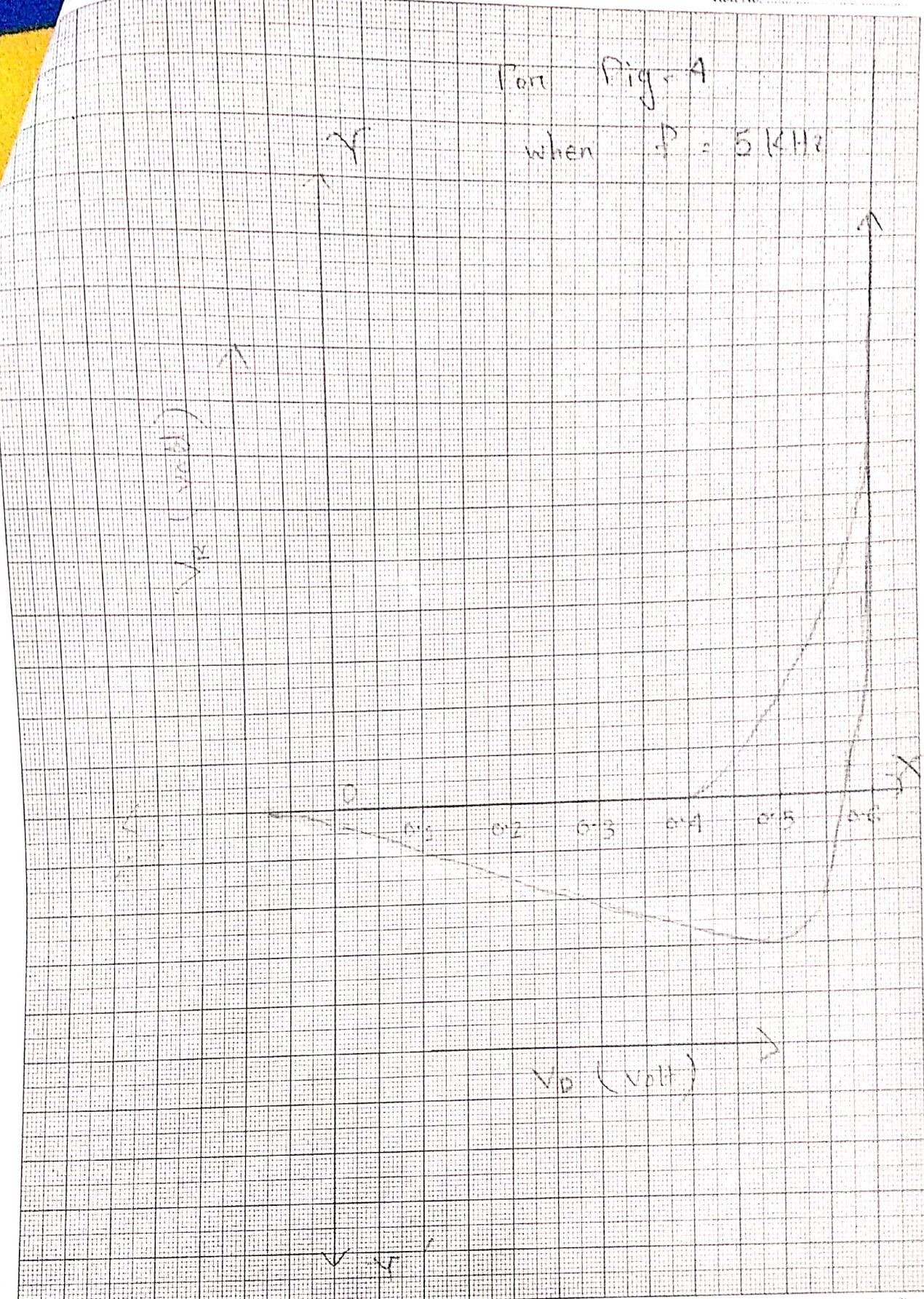when $P = 5 \text{ kPa}$ 

$$\text{D.R.}, "d = \frac{10000}{10 \times 10^{-3}} = (2.6 \times 10^4) - 1$$

2/

Calculate static and dynamic resistance

for $I_D = 5 \text{ mA}, 10 \text{ mA}$ and also for

$$V_D = 6.6 \text{ V}, 0.72 \text{ V} \quad \text{for circuit}$$

in Fig-2

Solution:

We know,

know ,
Static resistance , $R_D = \frac{V_D}{I_D}$

and dynamic resistance, $\pi_d = \frac{n V_T}{I_D}$

where n is identity factor

$$\text{For } I_D = 5 \text{ mA and } V_D = 0.59 \text{ V}$$

$$S.R. , \quad n_D = \frac{0.59}{5 \times 10^{-3}} = 120 \text{ Hz}$$

$$D.R. , R_d = \frac{n \times 0.026}{5 \times 10^{-3}} = (5.2n) \Omega$$

For $I_D = 10 \text{ mA}$ and $V_D = 0.72 \text{ V}$

$$S.R., \quad R_D = \frac{0.72}{10 \times 10^3} = 72 \Omega$$

$$D.R., R_d = \frac{n \times 0.626}{15 \times 10^{-3}} = (2.6n) \Omega$$

When $V_D = 0.6 \text{ V}$, $I_D = 5.8 \text{ mA}$

$$\text{S.R.}, \quad r_D = \frac{0.6}{5.8 \times 10^{-3}} = 103.45 \Omega$$

$$\text{D.R.}, \quad r_d = \frac{n \times 0.026}{5.8 \times 10^{-3}} = (4.48n) \Omega$$

When $V_D = 0.72 \text{ V}$, $I_D = 10 \text{ mA}$

$$\text{S.R.}, \quad r_D = \frac{0.72}{10 \times 10^{-3}} = 72 \Omega$$

$$\text{D.R.}, \quad r_d = \frac{n \times 0.026}{10 \times 10^{-3}} = (2.6n) \Omega$$

3/

Determine the Q point for the circuit in fig-2 when $V_{dc} = 15 \text{ volt}$

Answer:

Here, $V_{dc} = 15 \text{ v}$

From the graph, $V_D = 0.7 \text{ V}$

Again,

For the circuit,

$$V_{dc} = V_R + V_D$$

$$\therefore V_{dc} = IR + V_D$$

Now, $V_D = 0\text{ V}$ and $V_{dc} = 13\text{ V}$

$$\therefore I = 15\text{ mA}$$

From the graph,


the intersection point of the load

line and the curve is $(0.57, 2.4)$

So, the Q point is $(0.57, 2.4)$

5 cm

No. determine C point

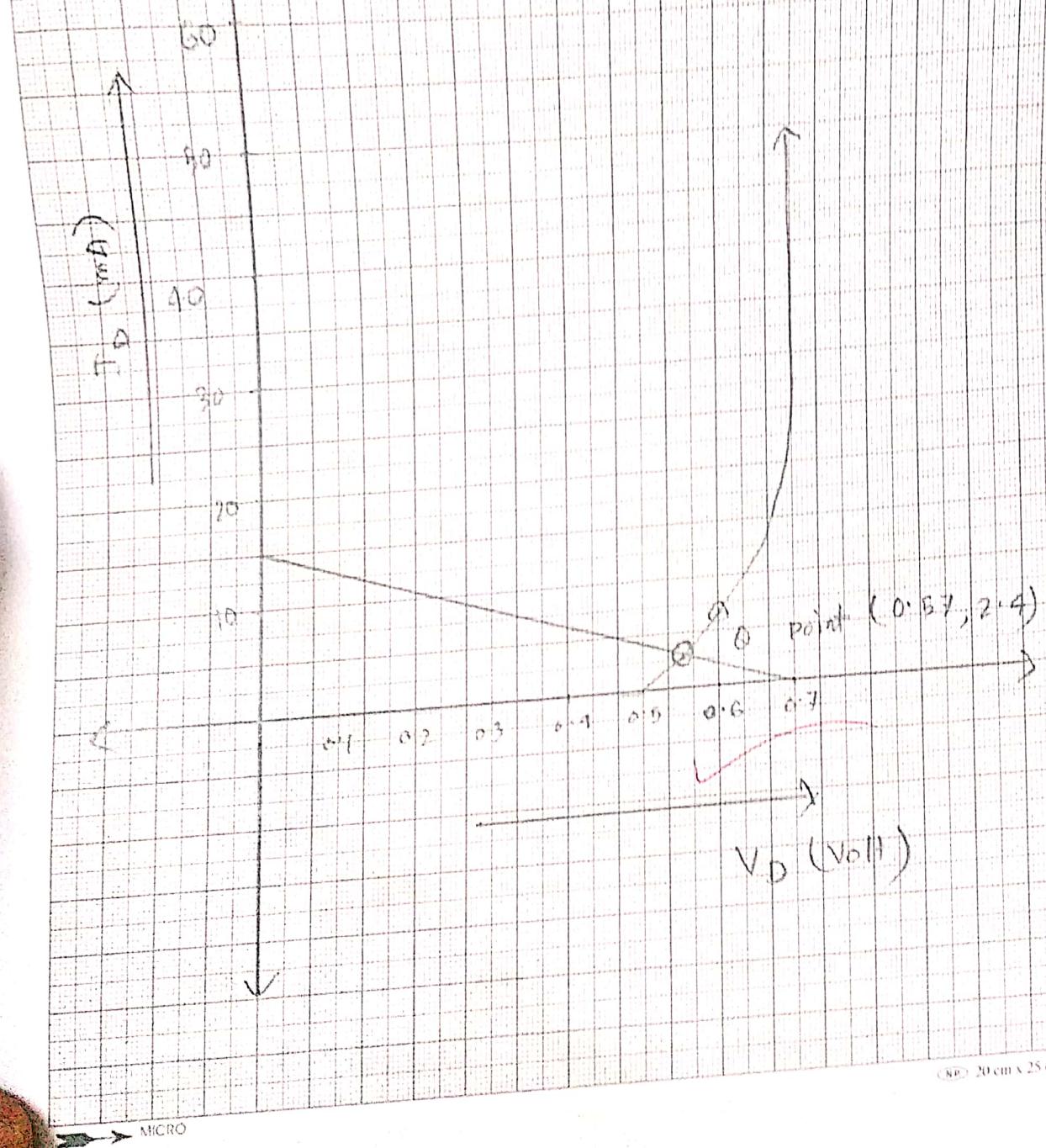

we can see a loop.

A/

Explain the result obtained in
Step - 4.

Answer :

At Step - 4, the basic difference we can see from Step - 3 is a loop.

During this step we apply high frequency input voltage. Because of that high frequency the electrons can not be stopped immediately after the operation turns off. That is why, the current starts to flow in the opposite direction. This is known as reverse recovery time. That is why, we can see a loop.

5/ What is the Zener voltage of the diode in Fig. 3?

Ans.

The voltage that is sufficient for the reverse breakdown condition, is known as Zener Voltage. It allows the diode to conduct in the reverse direction. From the graph and data table, we can see that the current is negligible during 0.5 volt to 5.1 volt. But when the voltage is 5.15 a huge amount of current starts to flow. So we can say that after 5.1 volt, the reverse breakdown condition occurs. So, the zener voltage of the diode in Fig-3

is 5.1 volt

6/

What is the dynamic resistance of the zener diode at zener voltage?

Answer:

The resistance which is offered by the p-n junction diode when AC voltage is applied is known as dynamic resistance.

The dynamic resistance can be measured by $\frac{dV}{dT}$. At zener voltage which is near to zero because the current flow is very high at that time. The voltage becomes very small comparing to the current. So $\frac{dV}{dT} \approx 0$. So, dynamic resistance is zero.